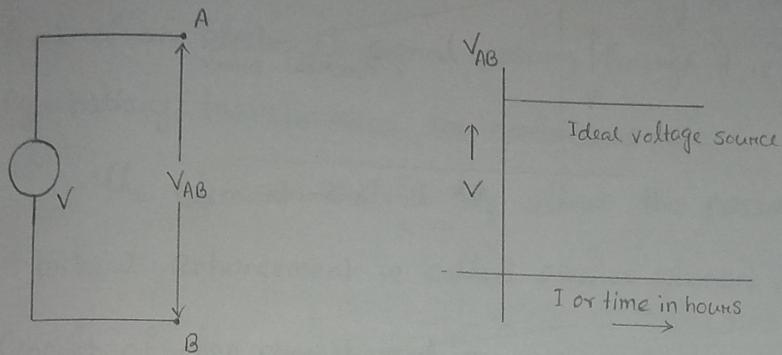


Module 1
DC circuits


I. Voltage and current sources -

1) Characteristics of ideal voltage and current sources:

i) In an ideal voltage source, the terminal voltage of the source is constant, whereas current drawn from the source can vary depending upon the connected load. An ideal voltage source has zero internal resistance and can never be short circuited.



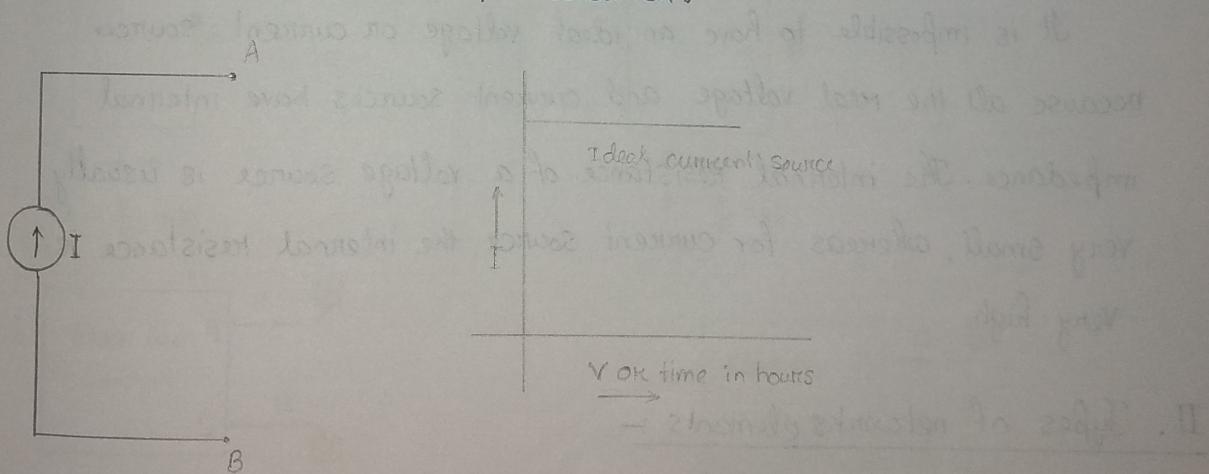ii) An ideal current source delivers constant current into the circuit, whereas the voltage across the ideal current source varies depending on the circuit parameters. An ideal current source has infinite internal resistance and can never be open circuited.




2) Independent voltage/current Sources:


The output voltage/current of an independent voltage/current source does not depend on any circuit element.

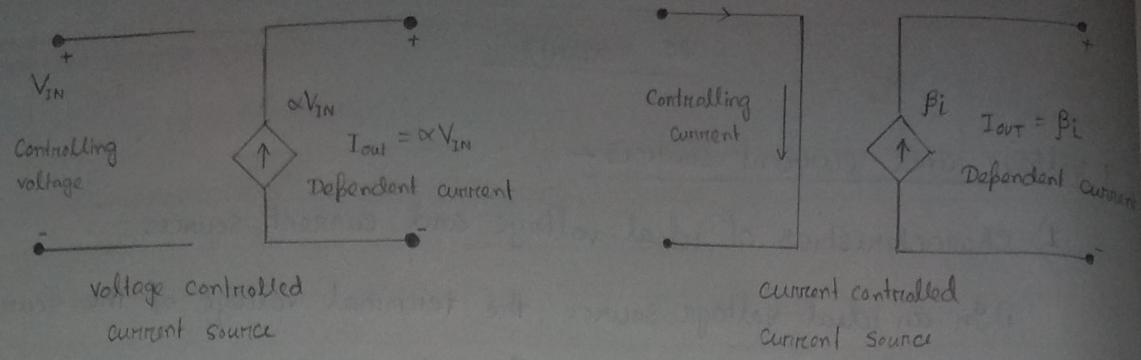3) Dependent or controlled sources:

The output depends on some other variables (voltage or current) in a circuit.



4) Practical voltage and current Sources

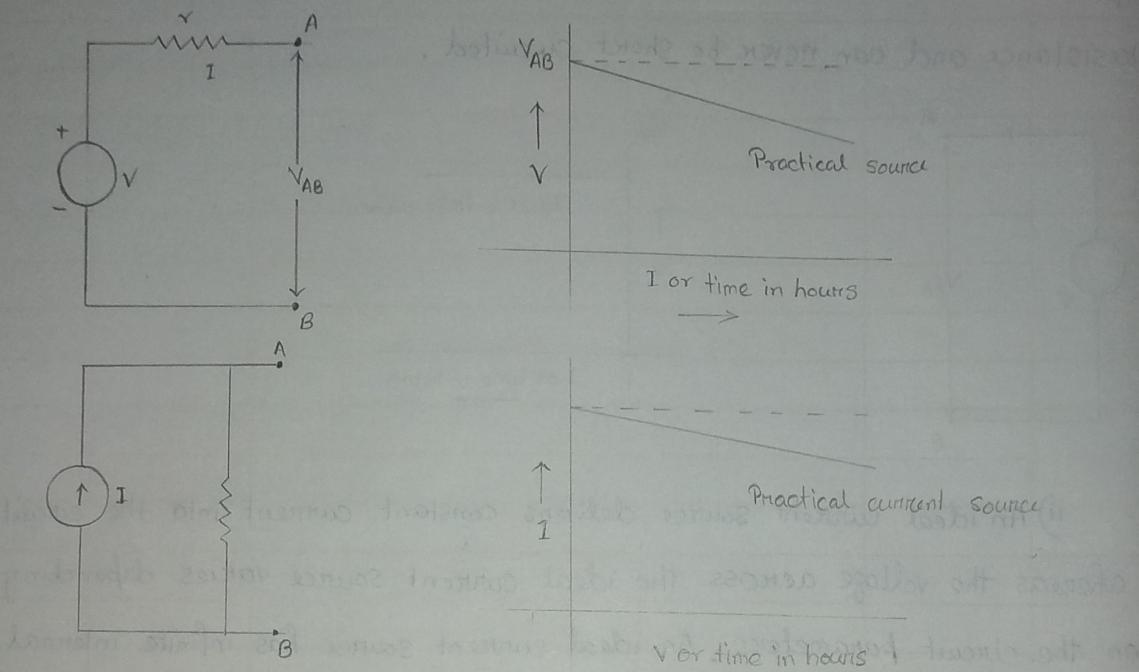

It is impossible to have an ideal voltage or current source because all the real voltage and current sources have internal impedance. The internal resistance of a voltage source is usually very small, whereas for current source, the internal resistance is very high.

II. Types of networks & elements :-

1) Linear and non-linear networks elements:-

A ^{element} network is said to be linear if it shows linear characteristics of voltage vs current. Eg - Resistors, inductors, capacitors etc.

A ^{element} network is said to be non-linear if its elements parameters change with applied voltage and current change. Eg - Semiconductor diodes devices like diodes, transistors, thyristors etc.

A non-linear network does not follow Ohm's law.

2) Unilateral and bilateral elements networks elements:

If the magnitude of the current passing through an element is affected due to change in polarity of the applied voltage, the element network is called unilateral network element.

If the current magnitude remains the same even if the polarity of the applied voltage is reversed, it is called bilateral element.

3) Active and passive networks (lumped and distributed networks)


If a circuit network has the capability of enhancing the energy level of an electrical signal passing through it, it is called an active element.

Eg - battery, transformers, semiconductors etc.

The element that simply allows the passage of the signal through it without enhancement is called passive element. Eg - resistors, inductors etc.

III. Concept of open circuit and short circuit:-


Open circuit

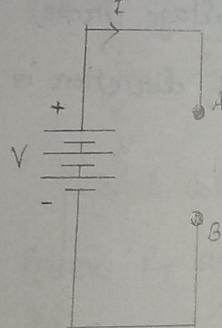

$$R \rightarrow \infty$$


$$I = \frac{V}{R} = 0$$

Short circuit


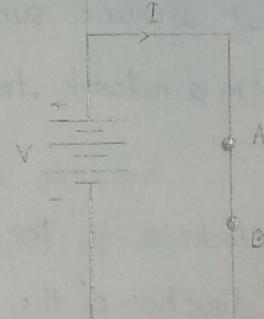


$$R \rightarrow 0$$


$$I = \frac{V}{R} = \infty$$

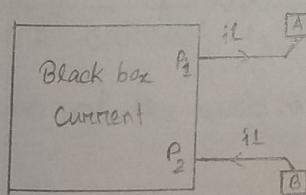

$$i_1 = 0$$

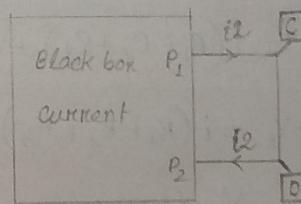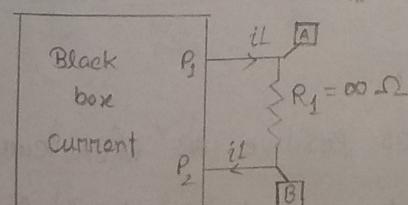

$$\nabla_{CD} = 0$$

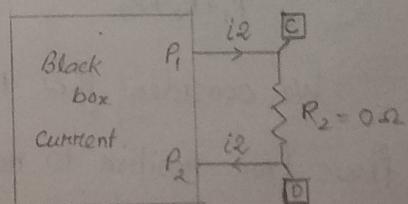

IV. Kirchhoff's law:

1) Kirchhoff's current law (KCL)

It states that in any electrical network the algebraic sum of currents meeting at any node of a circuit is zero.

Eg - Here i_1 and i_2 are the inward current towards the junction o and are assumed as negative currents. Currents i_3, i_4 and i_5 are outward current and are taken as positive. As per KCL

$$-i_1 - i_2 + i_3 + i_4 + i_5 = 0$$

$$\Rightarrow i_1 + i_2 = i_3 + i_4 + i_5$$


\therefore The algebraic sum of currents entering a node must be equal to the algebraic sum of currents leaving that node.

2) Kirchhoff's voltage law (KVL)

It states that algebraic sum of voltages (or voltage drops) in any closed path, in a network, traversed in a single direction is zero.

If we travel clockwise in the network along the direction of the current, application of KVL yields.

$$-V_1 + iR_1 + V_2 + iR_2 + iR_3 = 0$$

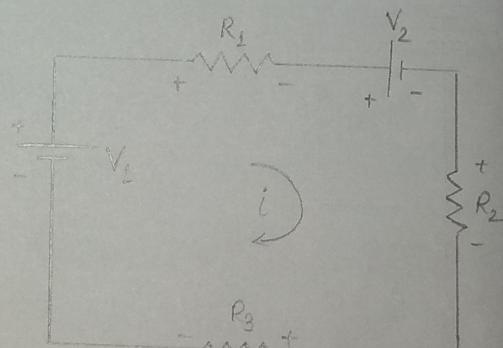

$$\Rightarrow V_1 = i(R_1 + R_2 + R_3) + V_2$$


$$\Rightarrow V_1 - V_2 = i(R_1 + R_2 + R_3)$$

$$\Rightarrow i = \frac{V_1 - V_2}{R_1 + R_2 + R_3}$$


We consider that the voltage drop is positive as when current flows from positive to negative potential. Hence V_1 is negative while V_2 is positive in the first step of equation.

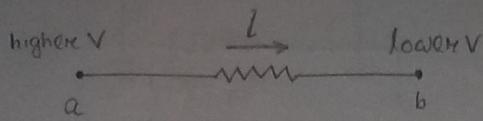V. Sign Convention -


Travel direction is always from left to right.




$$\Delta V = V_b - V_a = -IR$$

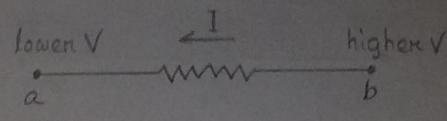

$$\Delta V = V_b - V_a = IR$$

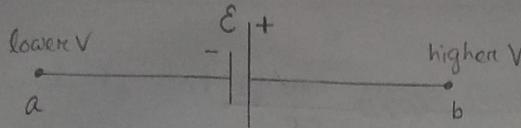

$$\Delta V = V_b - V_a = +E$$

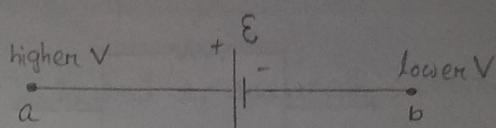

$$\Delta V = V_b - V_a = -E$$

Voltage division and current division


A set of two or more series connected resistors is frequently referred to as a voltage divider.

From Ohm's law,

$$\frac{V_j}{V_K} = \frac{I R_j}{I R_K} = \frac{R_j}{R_K}$$

$$\frac{P_j}{P_K} = \frac{I^2 R_j}{I^2 R_K} = \frac{R_j}{R_K}$$

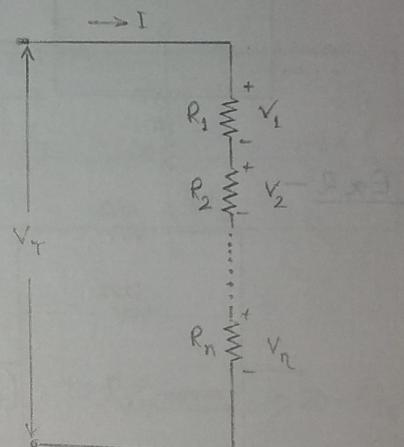
Total voltage V_T and total absorbed power P_T are divided in the ratio of the resistances



Two or more resistors on a parallel connection will divide the total current I_T and the total absorbed power P_T in the inverse ratio of the resistances.

$$\frac{I_j}{I_K} = \frac{V/R_j}{V/R_K} = \frac{R_K}{R_j}$$

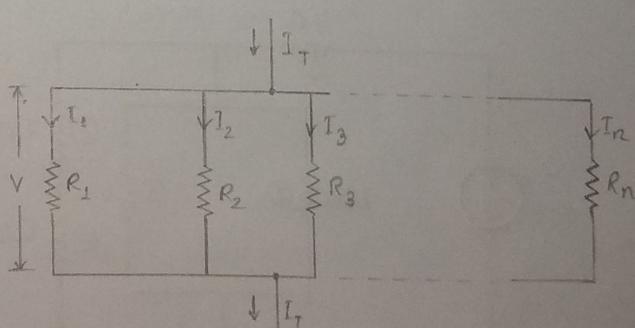
$$\frac{P_j}{P_K} = \frac{V^2/R_j}{V^2/R_K} = \frac{R_K}{R_j}$$



In Particular for $n=2$

$$I_1 = \frac{R_2}{R_1 + R_2} I_T, P_1 = \frac{R_2}{R_1 + R_2} P_T$$
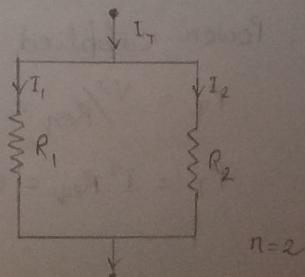
$$I_2 = \frac{R_1}{R_1 + R_2} I_T, P_2 = \frac{R_1}{R_1 + R_2} P_T$$




Series - Parallel network Reduction -

* For two series circuit elements :




* From two parallel circuit elements :

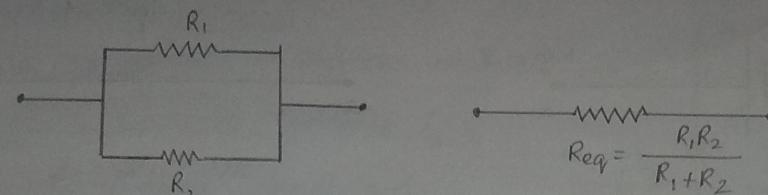


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


Ex 1 - What is the equivalent resistance if two 10Ω resistors connected in parallel.

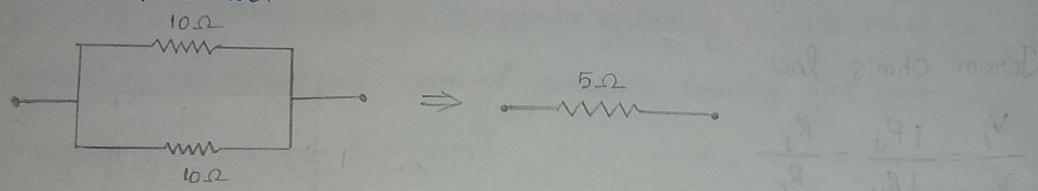

Ex 2 -

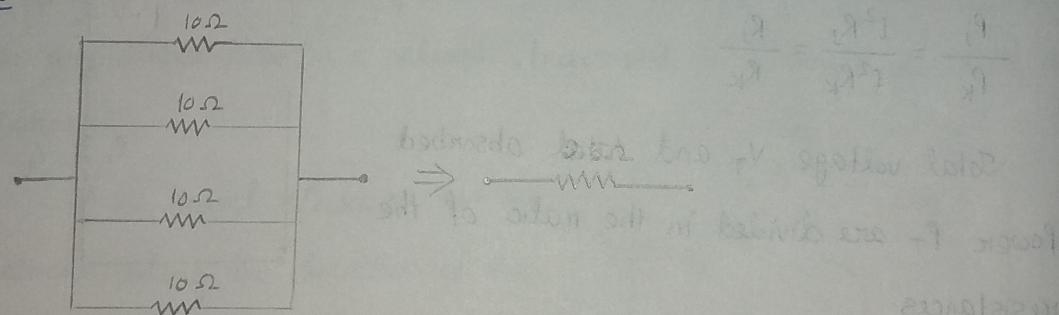

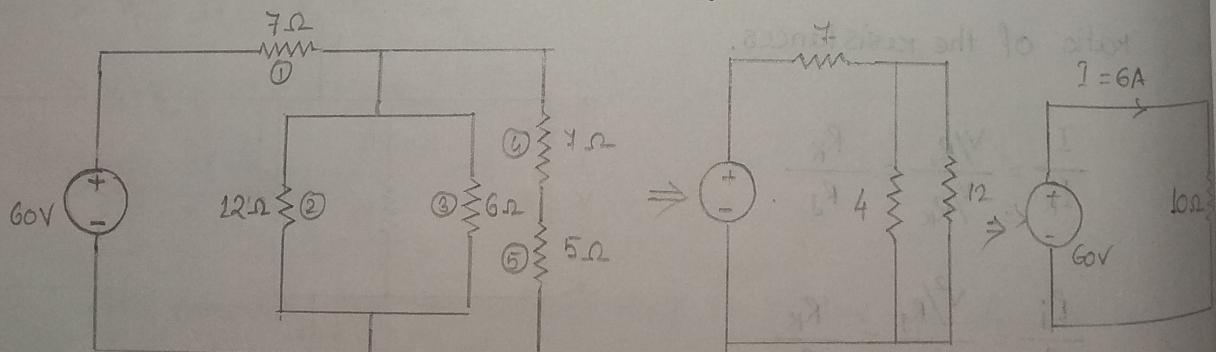Ex 3 - Obtain the total power supplied by $60V$ source and the power absorbed in each resistor in the network.



. Power supplied by the source

$$P_T = \frac{V^2}{R_{eq}} = \frac{60^2}{10} = 360W$$

$$P_T = I^2 R_{eq} = 6^2 \times 10 = 360W$$

$$\textcircled{1} \Rightarrow 4 \times 6^2 = 252W$$

$$\textcircled{2} \Rightarrow 18 \times 12 = 27W$$

$$\textcircled{3} \Rightarrow 18 \times 6 = 54W$$



$$\textcircled{4} \Rightarrow 7 \times 1.5^2 = 15.75W$$

$$\textcircled{5} \Rightarrow 5 \times 1.5^2 = 11.25W$$

Power absorbed

in each resistors.


DC meshes and node analysis

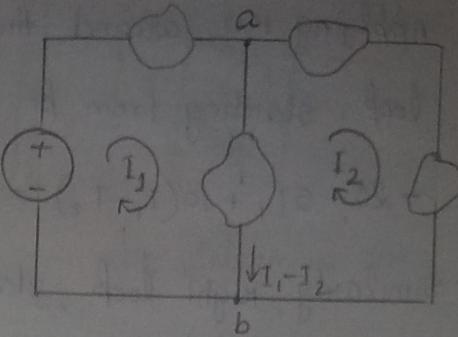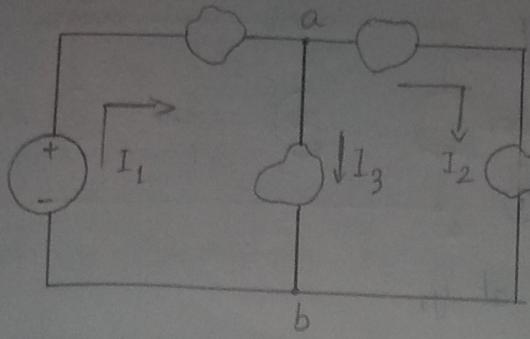

I_1, I_2 and I_3 are branch current

I_1 and I_2 are mesh current.

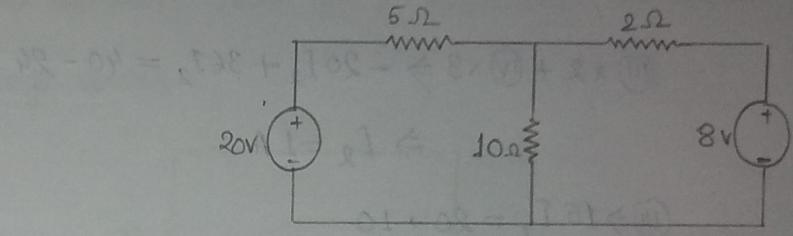Ex- solve the network by the (a) branch current and (b) Mesh current method.




Solⁿ a) Branch current method

Applying KCL at node 'a'

$$I_1 = I_2 + I_3 \quad \text{--- (1)}$$

Applying KVL to the left loop and

right loop wrt voltage, V_{ab}

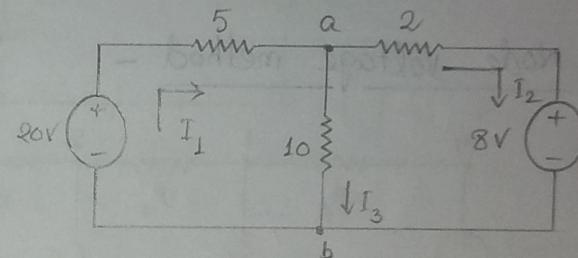

$$20 - 5I_1 = 10I_3 \quad \text{--- (II)} \Rightarrow 20 - 5(I_2 + I_3) = 10I_3 \Rightarrow 20 - 5I_2 = 15I_3 \quad \text{--- (II)}$$

$$20 - 5I_1 = 2I_2 + 8 \quad \text{--- (III)} \Rightarrow 20 - 5(I_2 + I_3) = 2I_2 + 8 \Rightarrow 12 - 7I_2 = +5I_3 \quad \text{--- (III)}$$

$$\text{Now, } (II) - 3(III) \Rightarrow 2I_2 + 8 = 10I_3$$

$$(II) - 3(III) \Rightarrow 20 - 5I_2 - 36 + 21I_2 = 0$$

$$\Rightarrow 16I_2 = 16$$

$$\Rightarrow I_2 = 1$$

$$(III) \Rightarrow 5I_3 = 12 - 7 \times 1$$

$$\Rightarrow I_3 = 1$$


$$(I) \Rightarrow I_1 = 1 + 1 = 2$$

$$\therefore I_1 = 2A, I_2 = 1A, I_3 = 1A$$

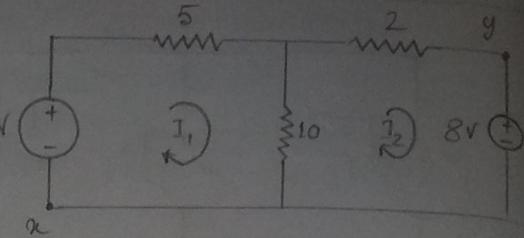b) Mesh current method

Applying KVL around the left loop, starting from pt x.

$$-20 + 5I_1 + 10(I_1 - I_2) = 0 \quad \text{--- (1)}$$



Similarly, right loop, starting at y,

$$8 + 10(I_2 - I_1) + 2I_2 = 0 \quad \text{--- (2)}$$

$$(1) \Rightarrow 15I_1 - 10I_2 = 20 \quad (3) \quad 8 + 10I_1 + 12I_2 + 8 = 0 \quad (4)$$



$$(3) \times 2 + (4) \times 3 \Rightarrow -20I_2 + 36I_2 = 40 - 24$$

$$\Rightarrow I_2 = 1A$$

$$(3) \Rightarrow 15I_1 = 20 + 10$$

$$\Rightarrow I_1 = 2A$$

Node Voltage method -

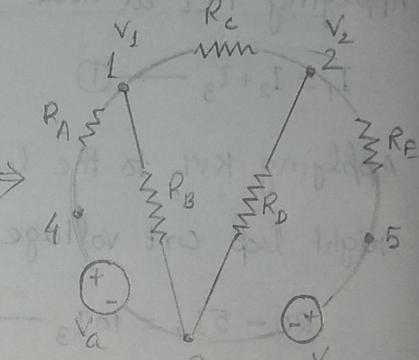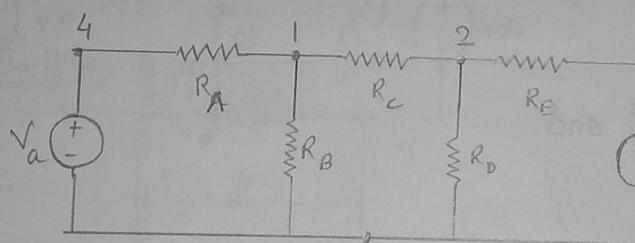

* Five nodes: 1, 2 and 4 are principal nodes

: 4 and 5 are simple nodes

: One of the principal nodes (node 3) is selected as reference node.

* Voltages are assigned at principal nodes except reference node and voltages are considered w.r.t reference node.

* Applying KCL at principal nodes we have

$$\text{At node 1: } \frac{V_1 - V_a}{R_A} + \frac{V_1}{R_B} + \frac{V_1 - V_2}{R_C} = 0 \quad \text{--- (1)}$$

$$\text{At node 2: } \frac{V_2 - V_1}{R_C} + \frac{V_2}{R_D} + \frac{V_2 - V_b}{R_E} = 0 \quad \text{--- (2)}$$

where V_1 and V_2 are two unknowns.


In matrix form:

$$\begin{bmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_a/R_A \\ V_b/R_E \end{bmatrix}$$

Solving the matrix for V_1 and V_2 , we can determine the values of branch currents.

Ex 1 - Calculate the internal resistance of a battery which has an open circuit voltage 12V and delivers 100A to a resistance of 0.1Ω .

Solⁿ: It is a practical voltage source.

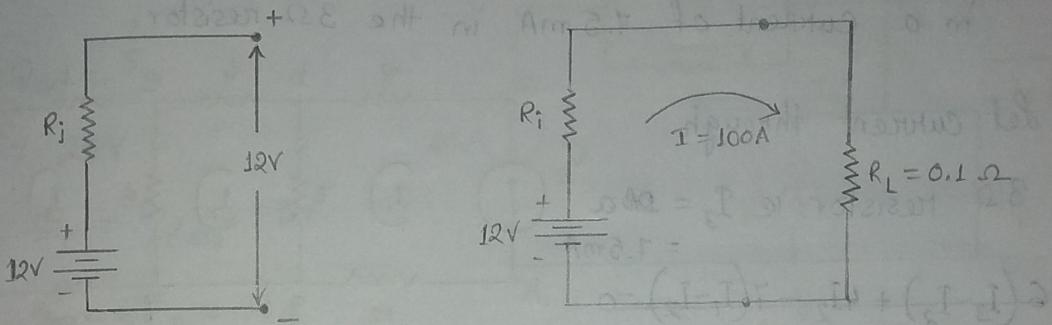

$$I = 100A = \frac{12}{0.1 + R_i} \Rightarrow R_i = 0.02\Omega$$

Ex 2 Measurements made on a practical DC source show a terminal voltage of 100V for a load resistance of 100Ω and 105V for a resistance of 210Ω . Calculate the source voltage and internal resistance.

Solⁿ Given $E_1 = 100V$, $R_1 = 100\Omega$

$$E_2 = 105V, R_2 = 210\Omega$$

Let the internal resistance be r .

(From Ohm's law, we say, $E = I(R+r)$)

$$100 = I(100+r) \quad \text{--- (i)}$$

$$105 = I(210+r) \quad \text{--- (ii)}$$

$$\text{Now, } \frac{(i)}{(ii)} \Rightarrow \frac{100}{105} = \frac{100+r}{210+r}$$

$$\Rightarrow 21000 + 100r = 10500 + 105r$$

$$\Rightarrow 10500 = 5r \Rightarrow r =$$

$$R_{eq} = \frac{Rr}{R+r}$$

$$E = I R_{eq}$$

$$\therefore 100 = I \cdot \frac{100r}{100+r} \quad \text{--- (i)}$$

$$105 = I \cdot \frac{210r}{210+r} \quad \text{--- (ii)}$$

$$\text{Now, } \frac{(i)}{(ii)} \Rightarrow \frac{100}{105} = \frac{100r(210+r)}{210r(100+r)}$$

$$\Rightarrow 200 + 2r = 210 + r$$

$$\Rightarrow r = 10$$

$$\therefore V = I \frac{100 \times 10}{100 + 10} \quad \therefore V = I(R+r)$$

$$\Rightarrow V = \frac{100}{11} I$$

$$E = I R_{\text{eq}}$$

$$\Rightarrow I = \frac{E}{R_{\text{eq}}} = \frac{100}{\frac{100}{11}} = \frac{28}{20} A = 1.4 A$$


$$V = I r = 1.4 \times 10 = 14 V$$

Ex 3 - In the network find the source voltage V_s which results in a current of 7.5 mA in the 3Ω resistor.

Soln Let current through

$$3\Omega \text{ Resistor ie } I_3 = 7.5 \text{ mA}$$
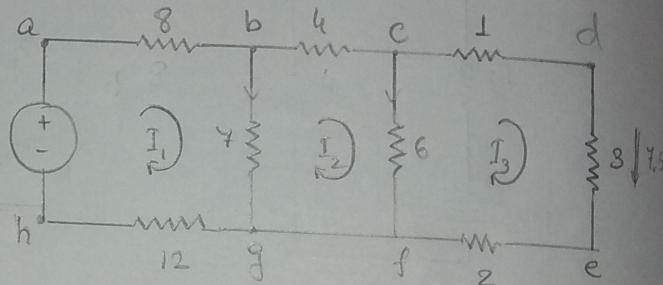
$$6(I_3 - I_2) + 4I_2 - 7(I_1 - I_2) = 0$$



~~By applying KCL on loop bcfq, we get~~

~~$$6(I_3 - I_2) + 4I_2 - 7(I_1 - I_2) = 0$$~~

~~$$6I_3 + 5I_2 - 7I_1 = 0$$~~

~~$$7I_1 - 5I_2 = 6 \quad \dots \textcircled{1}$$~~

By applying KCL on loop bedf, we get

$$2I_3 + 8I_3 + I_3 = 6(I_2 - I_3)$$

$$12I_3 = 6I_2$$

$$I_2 = 2I_3 = 2a$$

By applying KCL on loop befg, we get

$$6(I_2 - I_3) + 4I_2 = 7(I_1 - I_2)$$

$$17I_2 = 7I_1 + 6I_3$$

$$34a - 6a = 7I_1 \Rightarrow I_1 = \frac{28}{7}a = 4a$$

Applying KVL on loop abgh, we get,

$$12I_1 + 7(I_1 - I_2) + 8I_1 = V_s$$

$$\Rightarrow V_s = 27I_1 - 7I_2$$

$$= 108A - 14A$$

$$= 94A$$

$$= 94 \times 7.5 \times 10^{-3} V$$


$$= 0.705 V.$$

Ex 4 - Obtain the current in each resistor using network reduction method.

Soln $R_{eq} = 5$

$$V = 25V$$

$$\therefore I_T = V/R_{eq} = 5A$$

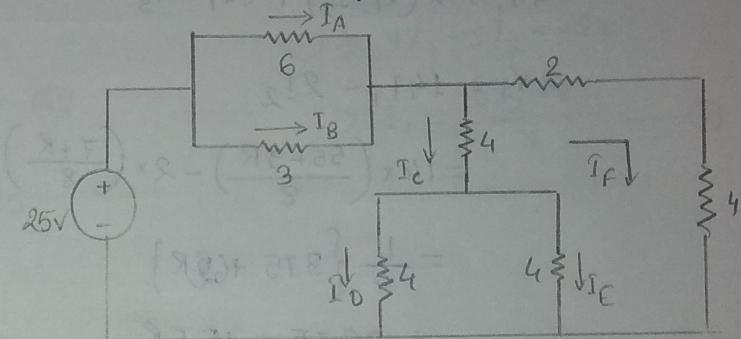

$$I_D = 6I_A = 3I_B$$


$$\Rightarrow I_B = 2I_A$$

$$\therefore I_B = \frac{5}{3} A$$

$$I_A = \frac{10}{3} A$$

$$I_C = I_F = \frac{5}{2} A = 2.5A$$

$$I_D = I_E = \frac{5}{4} A = 1.25A.$$

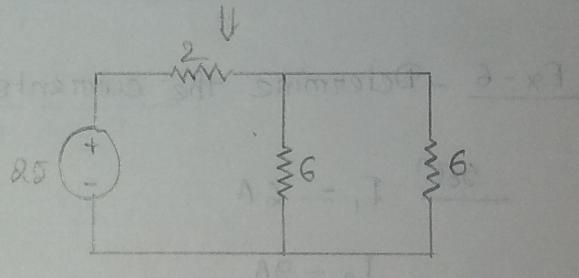


Ex 5 - Find the value of the source voltage V_s if power dissipated in the 3Ω resistor is $0.75W$.

Doubt: Soln $8I_3^2 = P_{3\Omega} = 0.75W$

$$\Rightarrow 8I_3^2 = 0.75$$

$$\Rightarrow I_3^2 = 0.25$$
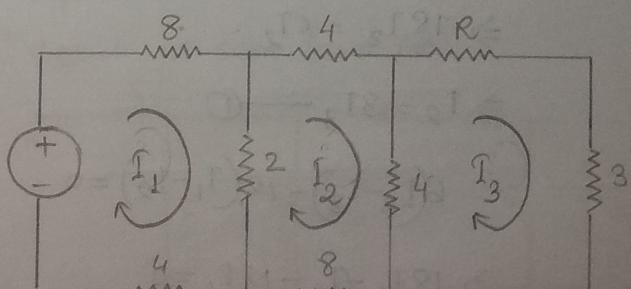
$$\Rightarrow I_3 = 0.5A = \frac{1}{2}A$$



We will By applying Kirchhoff's law on the ckt, we get

$$8I_3 + RI_3 = 4(I_2 - I_3)$$

$$\Rightarrow (7+R)I_3 = 4I_2 \Rightarrow I_2 = \left(\frac{7+R}{8}\right)A$$

$$8I_2 + 4(I_2 - I_3) + 4I_2 = 2(I_1 - I_2)$$

$$\Rightarrow 18I_2 - 4I_3 = 2I_1$$

$$\Rightarrow 2I_1 = \frac{7+R}{8} \times 18 - 4 \times \frac{1}{2}$$

$$\Rightarrow 2I_1 = \frac{9(7+R)}{4} - 2$$

$$\Rightarrow 2I_1 = \frac{55+9R}{4}$$

$$\Rightarrow I_1 = \left(\frac{55+9R}{8}\right) A$$

And, $4I_1 + 2(I_1 - I_2) + 8I_1 = V_s$

$$\Rightarrow V_s = 14I_1 - 2I_2$$

$$= 14 \times \left(\frac{55+9R}{8}\right) - 2 \times \left(\frac{7+R}{8}\right)$$


$$= \frac{1}{4} \{ 375 + 68R \}$$

$$= 93.75 + 15.5R$$

Ex-6 - Determine the currents I_1 and I_2

Soln $I_1 = -6A$

$$I_2 = 9A$$

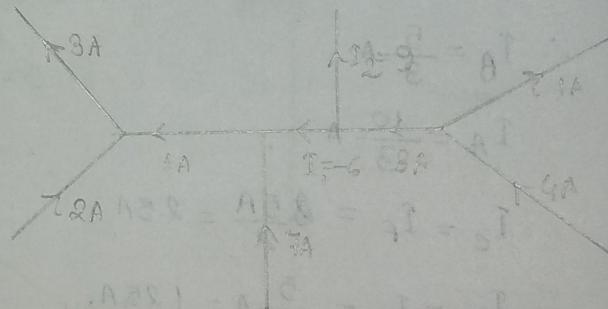

Ex-7 - Solve the network using mesh current method

Soln $12I_3 - 6(I_2 - I_3) = 0$

$$\Rightarrow 18I_3 = 6I_2$$

$$\Rightarrow I_2 = 3I_3 \quad \text{(1)}$$


$$6(I_2 - I_3) - 12(I_1 - I_2) = 0$$

$$\Rightarrow 18I_2 - I_3 - 12I_1 = 0$$

$$\Rightarrow 12I_1 = 54I_3 - 6I_3$$

$$\Rightarrow 12I_1 = 48I_3$$
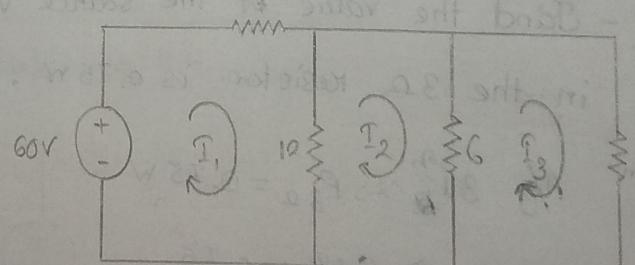
$$\Rightarrow I_1 = 4I_3 \quad \text{(2)}$$



$$12(I_1 - I_2) + 7I_1 = 60$$

$$\Rightarrow 19 \times 4I_3 - 12 \times 3I_3 = 60$$

$$\Rightarrow 40I_3 = 60$$

$$\Rightarrow I_3 = \frac{3}{2} = 1.5A$$

$$\therefore I_1 = 4 \times \frac{3}{2} = 6A \quad \& \quad I_2 = 3 \times \frac{3}{2} = 4.5A$$

Ex-8 solve the network using (a) mesh current method
 (b) Node-voltage method.

Soln a) Mesh current method

$$-50 + 4(I_3 - I_2) + 2I_3 = 0$$

$$\Rightarrow 6I_3 - 4I_2 = 50 \quad \text{--- (i)}$$

$$10I_2 + 4(I_2 - I_3) + 5(I_2 - I_1) = 25$$

$$\Rightarrow 19I_2 - 4I_3 - 5I_1 = 25 \quad \text{--- (ii)}$$

$$5(I_1 - I_2) + 25 + 2I_1 = 0$$

$$\Rightarrow 7I_1 - 5I_2 = -25 \quad \text{--- (iii)}$$

$$\text{--- (i)} \Rightarrow 2I_2 = 3I_3 - 25$$

$$\Rightarrow I_2 =$$

$$\text{--- (ii)} \Rightarrow 19I_2 - 4 \times \frac{25+2I_2}{3} - 5 \times \frac{5I_2 - 25}{7} = 25$$

$$\Rightarrow \left(19 - \frac{8}{3} - \frac{25}{7}\right)I_2 = 25 + \frac{100}{3} - \frac{125}{7}$$

$$\Rightarrow I_2 = \frac{40.4762}{12.7619} = 3.17 \text{ A}$$


$$I_1 = -1.31 \text{ A}$$

$$I_2 = 3.17 \text{ A}$$



$$I_3 = 10.45 \text{ A.}$$

Equivalent Resistance



Ex-1

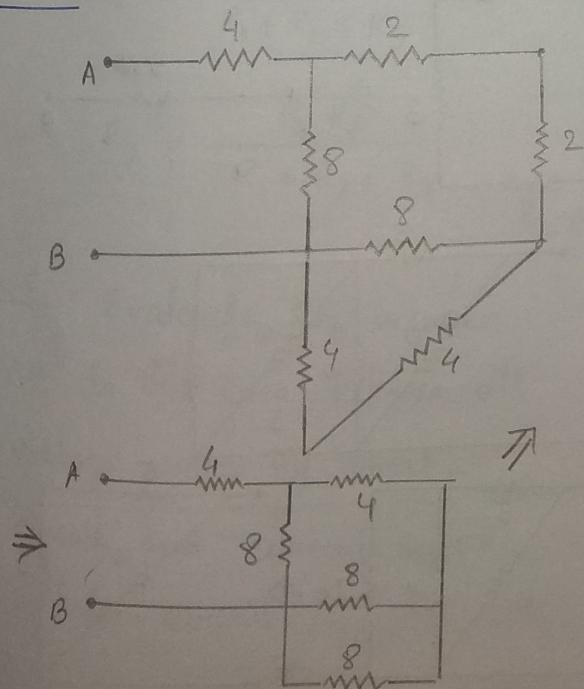



Equivalent resistance of the circuit as seen from AB.

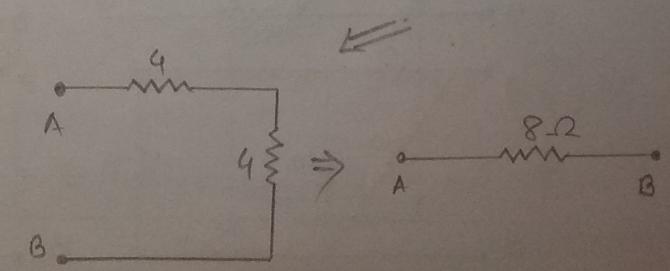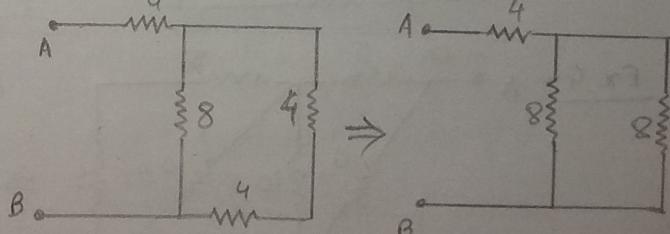



Ex 2 -


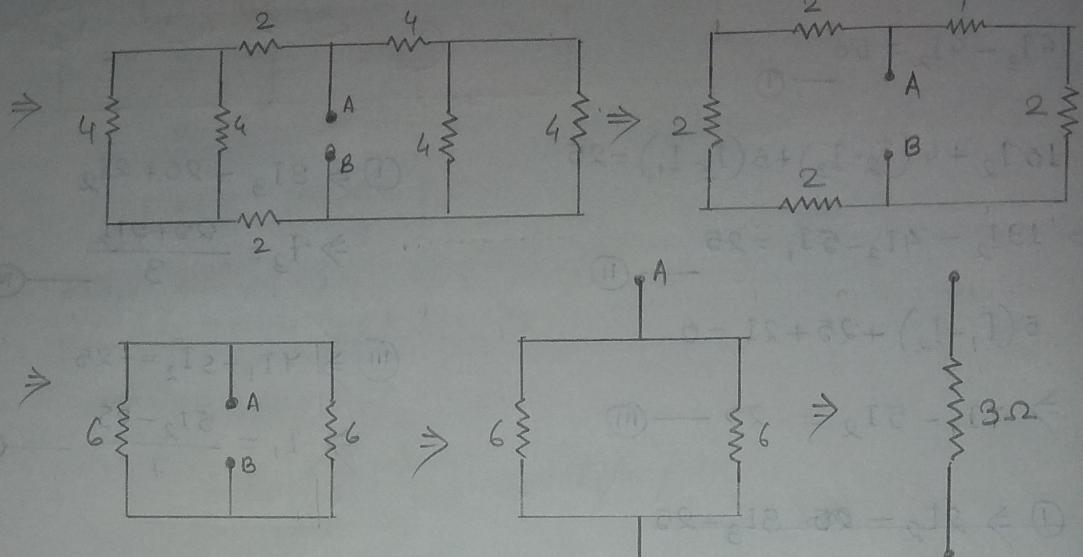
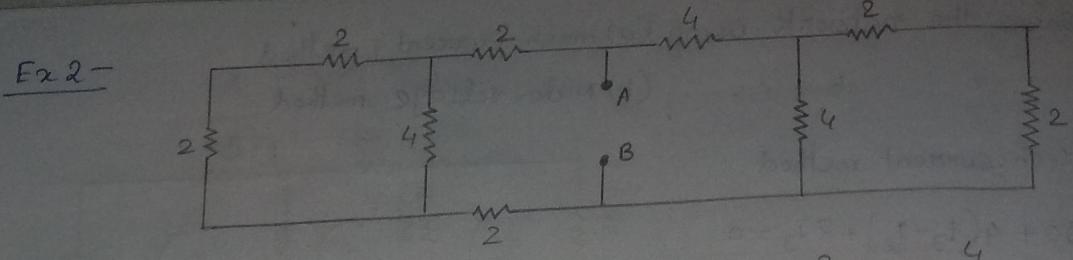


Ex 3 -

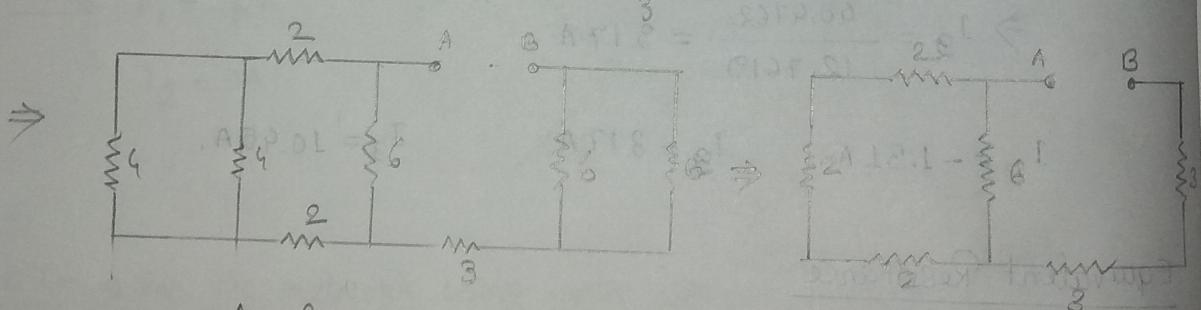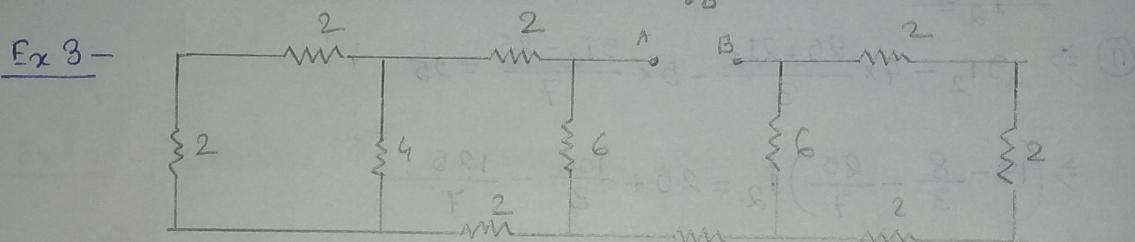

Ex 4 -

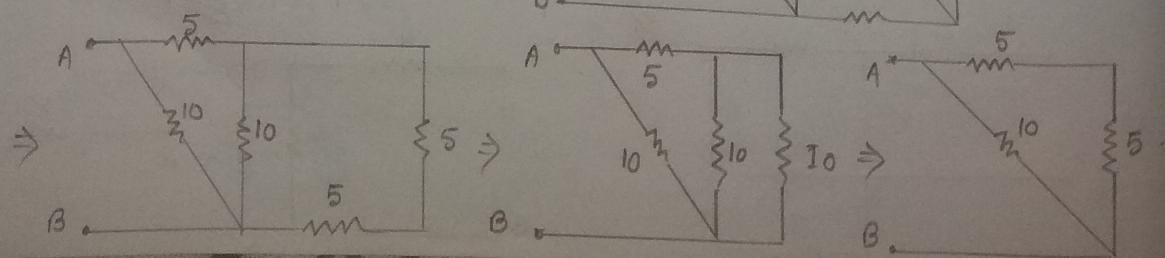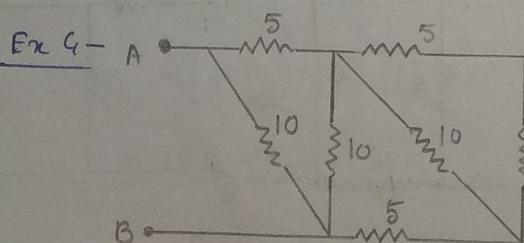

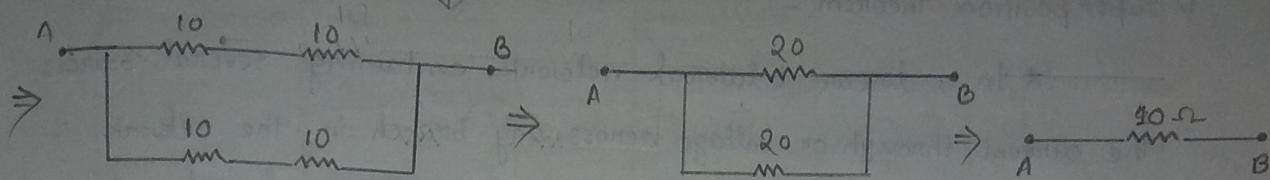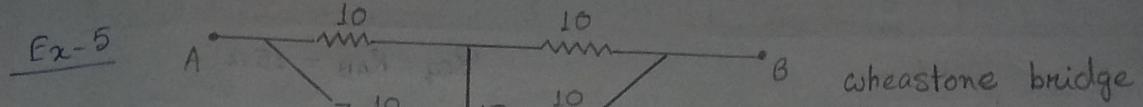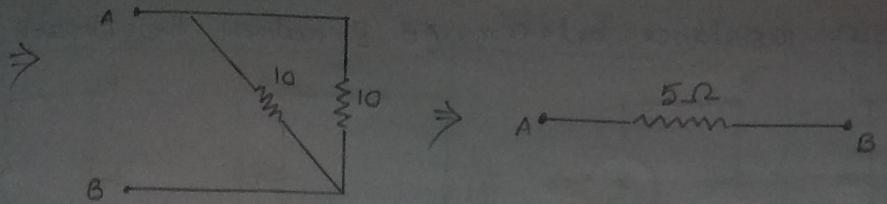


Star-Delta conversion -

Y-Δ Transformation - conversion of branch impedances

$$R'_1 = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R'_2 = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
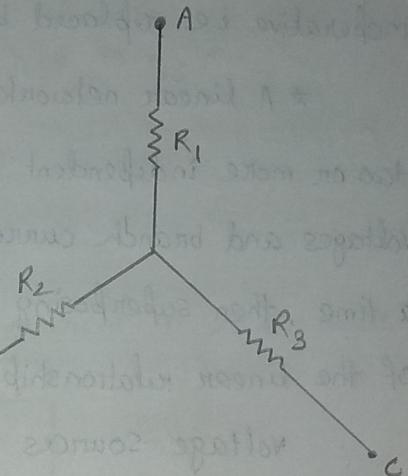
$$R'_3 = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$




Δ-Y Transformation - transformation of branch impedances

$$R_1 = \frac{R'_1 R'_3}{R'_1 + R'_2 + R'_3}$$

$$R_2 = \frac{R'_1 R'_3}{R'_1 + R'_2 + R'_3}$$

$$R_3 = \frac{R'_1 R'_2}{R'_1 + R'_2 + R'_3}$$

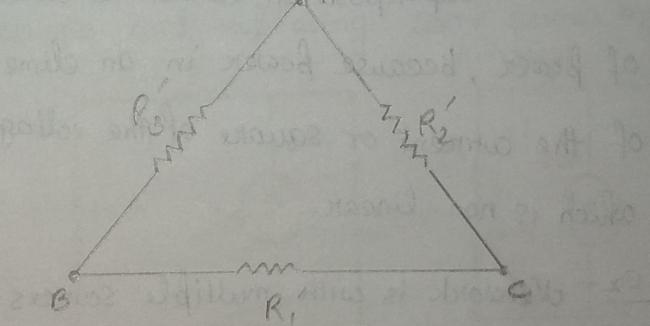


Ex 6 - Evaluate Req between

AB. In this case, replace all


voltage source by 'short-

circuit' and circuit source

by 'open-circuit.'

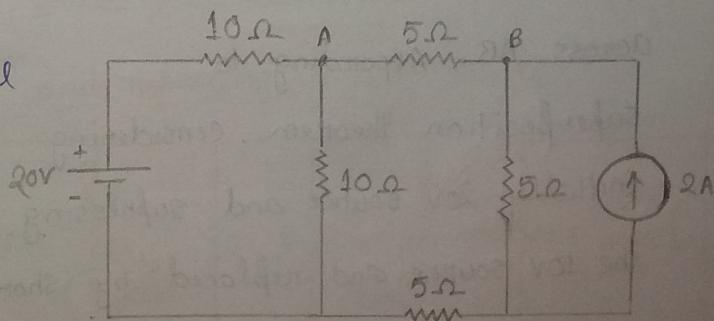

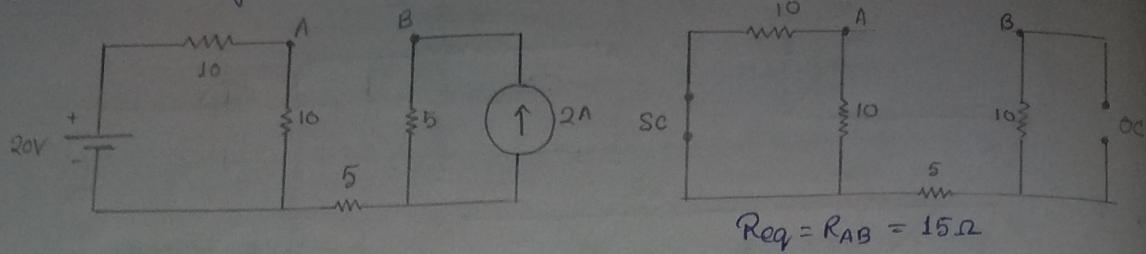Sol" Removing 5Ω resistance between AB & redraw the circuit.



Network Theorems -

1) Superposition theorem -

★ In a linear bilateral network containing several sources, the current through or voltage across any branch in the network equals the algebraic sum of the currents or voltages of each individual source considered separately with all other sources made inoperative i.e replaced by resistances equal to their internal resistances.

★ A linear network (eg. a DC resistive network) which contains two or more independent sources can be analyzed to obtain the various voltages and branch currents by allowing the sources to act one at a time, then superposing the results. This principle applies because of the linear relationship between current and voltage.

voltage sources to be suppressed while a single source acts are replaced by short circuits; current sources are replaced by open circuits.


Superposition cannot be directly applied to the computation of power, because power in an element is proportional to the square of the current or square of the voltage. (ie Power = $i^2 R$ or V^2/R), which is non-linear.


Ex- Network is with multiple sources.

Determine current in resistance 40Ω across AB. According to

superposition theorem, considering initially $20V$ source and suppressing

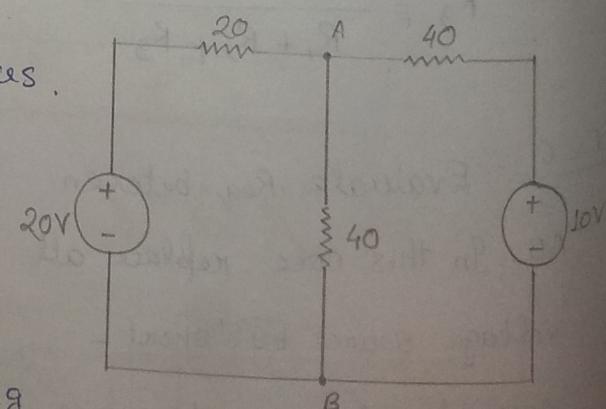
the $10V$ source and replaced by short circuit.



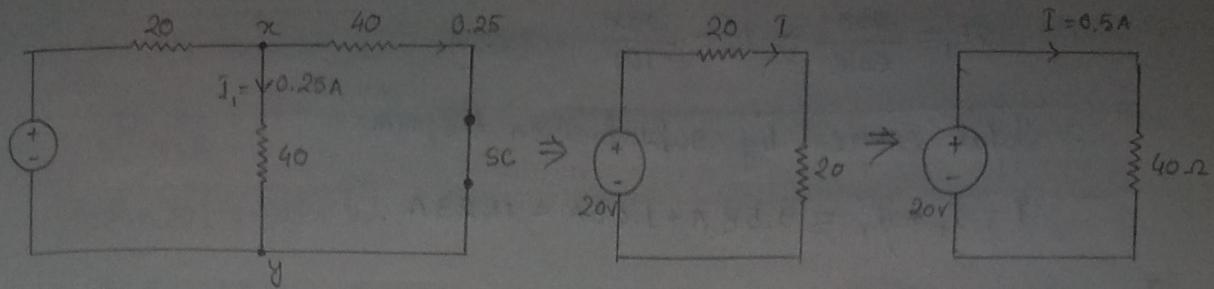

So, due to 20V source current in 40Ω resistor is $I_1 = 0.25\text{A}$ (x to y)

Next, considering 10V source only.

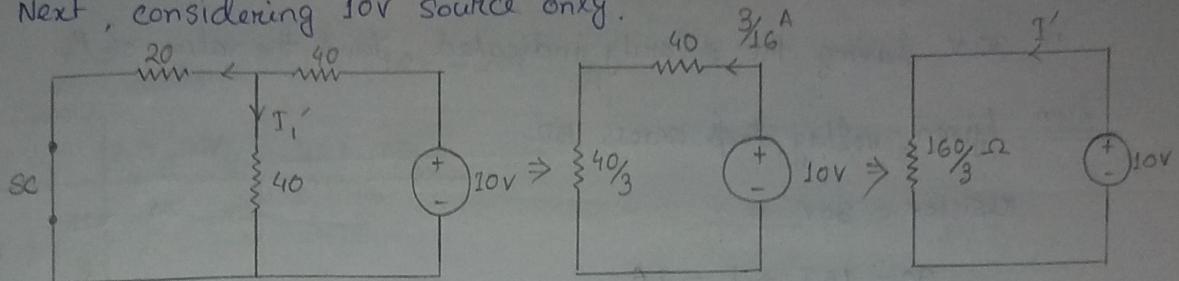


$$I' = \frac{10}{160/3} = \frac{30}{160} = \frac{3}{16}\text{A}, \quad I_1' = \frac{20}{20+40} \times \frac{3}{16} = \frac{20}{60} \times \frac{3}{16} = \frac{1}{16}\text{A}$$

\therefore Current in 40Ω when 10V is considered is $\frac{1}{16}\text{A}$


\therefore Total current by superposition theorem

$$I = I_1 + I_1' = \frac{1}{4} + \frac{1}{16} = \frac{4+1}{16} = \frac{5}{16}\text{A}$$

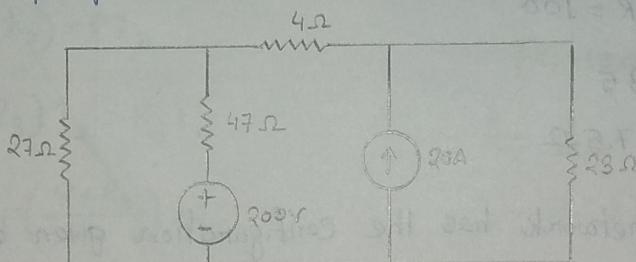Ex Apply superposition theorem to find current in 23Ω resistor.




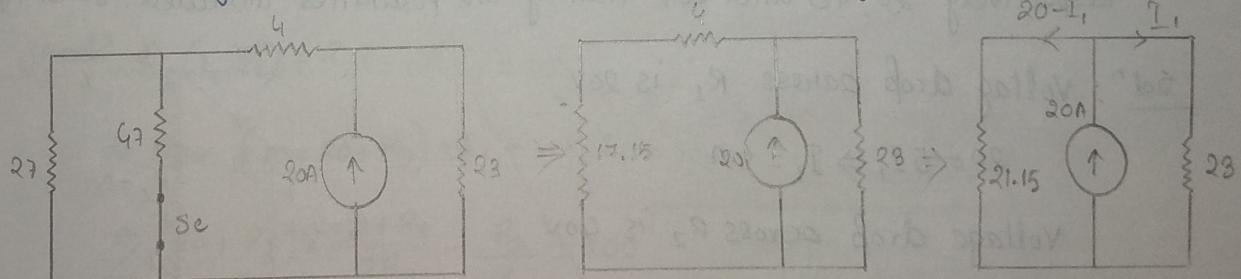Soln Considering 20A current source and replacing 200V source by SC.



$$21.15(20-I) = 23I_1 \Rightarrow 44.15I_1 = 423 \Rightarrow I_1 = 9.58\text{A}$$

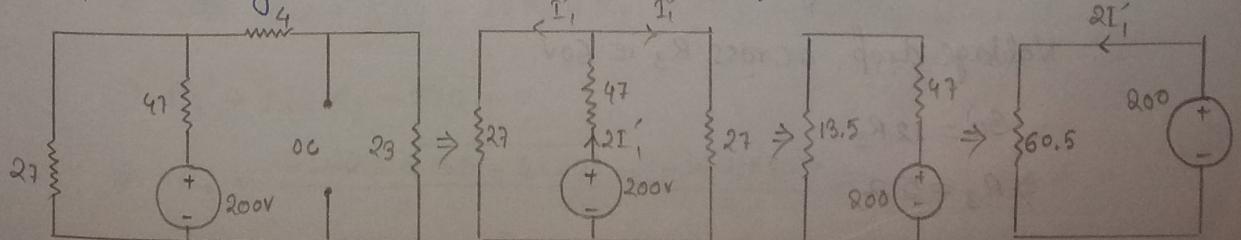Now, Considering 200V source and replacing 20A source by OC.



$$2I_1' = \frac{200}{60.5} \Rightarrow I_1' = \frac{200}{121} = 1.65A$$

\therefore Total current by superposition theorem

$$I = I_1 + I_1' = 9.58A + 1.65A = 11.23A.$$

Few more exercise \rightarrow

- 1) The voltage drop across the 15Ω resistance in the circuit of is $30V$ having the polarity indicated. Find the value of R .


Soln: Given, voltage drop across 15Ω

$$\text{resistor} = 30V$$

$$\therefore 30 = 15I_1 \Rightarrow I_1 = 2A$$

\therefore Current passing through 5Ω resistor

is $4A$ and through Resistor R is $2A$.

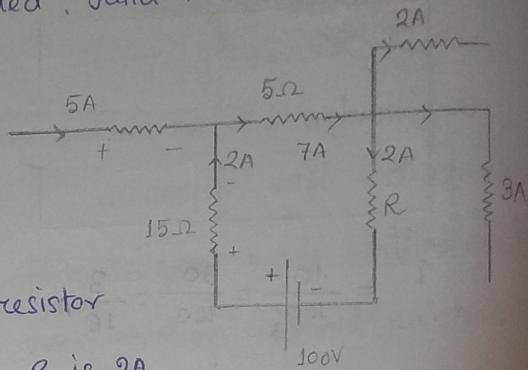

By applying KVL, we get

$$15 \times 2 + 5 \times 7 + 2R = 100$$

$$\Rightarrow 30 + 35 + 2R = 100$$

$$\Rightarrow 65 + 2R = 100$$

$$\Rightarrow 2R = 35$$

$$\Rightarrow R = 17.5\Omega$$

- 2) A portion ~~of~~ of a network has the configuration given below. The voltage drops existing across the three resistors are known to be respectively 20 , 40 and $60V$ having the polarities indicated. Find R_3

Soln: Voltage drop across R_1 is $20V$

$$20 = 5I_1 \Rightarrow I_1 = 4A$$

Voltage drop across R_2 is $40V$


$$40 = 20I_2 \Rightarrow I_2 = 2A$$

Current through R_3 is $I_3 = 10 + 4 - 2 = 12A$

Voltage drop across R_3 is $60V$

$$60 = 12R_3$$


$$\Rightarrow R_3 = 5\Omega$$

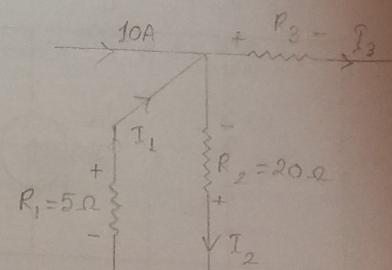

3) Find the voltage across AB

Solⁿ: Applying KVL, we get 2 eqns.

$$20V + 10I + 20I + 5I = 110$$

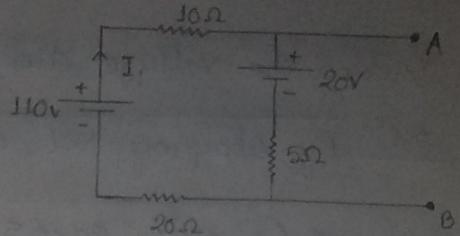

$$\Rightarrow 35I = 90$$

$$\Rightarrow I = \frac{18}{7} A$$

$$\text{And, } V_A - 10I + 110V - 20I = V_B$$

$$\Rightarrow V_A - V_B = 30I - 110$$

$$= \frac{540}{7} - 110$$

$$= \frac{-770 + 540}{7}$$

$$= \frac{230}{7} = 32.86 V$$

∴ The voltage across AB is 32.86 V.


4) Find the voltage drop across R_1 and R_2 . The resistance R_3 is not specified.

~~$$\text{Sol}^n R_3(I_1 - I_2) = 8I_2$$~~

~~$$\Rightarrow (8 + R_3)I_2 = R_3 I_1$$~~

~~$$\Rightarrow R_3 I_1 = \left(\frac{8 + R_3}{R_3} \right) \times 0.5$$~~

~~$$= \frac{8 + R_3}{2R_3}$$~~

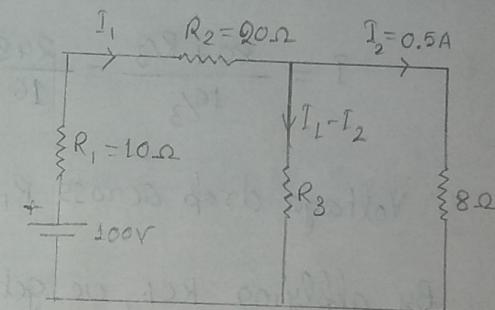

~~$$\text{And, } R_3(I_1 - I_2) + R_2 I_1 + R_1 I_1 = 100$$~~

~~$$\Rightarrow (10 + 20 + R_3) \times I_1 - R_3 I_2 = 100$$~~

~~$$\Rightarrow (30 + R_3) \times \frac{8 + R_3}{2R_3} - \frac{R_3}{2} = 100$$~~

~~$$\Rightarrow (30 + R_3)(8 + R_3) - 2R_3^2 = 200R_3$$~~

~~$$\Rightarrow 240 + 8R_3 + 30R_3 + R_3^2 - 2R_3^2 = 200R_3$$~~

~~$$\Rightarrow R_3^2 + 162R_3 - 240 = 0$$~~

~~$$R_3 = \frac{-162 \pm \sqrt{162^2 - 4 \times 240}}{2} = \frac{-162 + 159}{2} =$$~~

Q) Find the voltage drop across R_1 & R_2 . The resistance R_3 not specified.

Sol' By applying KCL, we get

$$R_3(I - 0.5) = 80 \times 0.5$$

$$\Rightarrow R_3 I - \frac{R_3}{2} = 40$$

$$\Rightarrow I = \frac{40 + \frac{R_3}{2}}{R_3} = \frac{80 + R_3}{2R_3}$$

By applying KVL, we get

$$R_3(I - 0.5) + R_2 \cdot 20I + 10I = 100$$

$$\Rightarrow R_3 \times \frac{80 + R_3}{2R_3} - \frac{R_3}{2} + 80 \times \frac{80 + R_3}{2R_3} = 100$$

$$\Rightarrow 80R_3 + R_3^2 - \frac{R_3^2}{4} + 240 + 30R_3 = 200R_3$$

$$\Rightarrow 90R_3 = 240$$

$$\Rightarrow R_3 = \frac{8}{3} = 2.66 \Omega$$

$$I = \frac{80 + \frac{8}{3}}{\frac{16}{3}} = \frac{248}{16} = 15.5 A$$

\therefore Voltage drop across R_1 is $10 \times 15.5 = 155 V$

By applying KCL, we get

$$R_3(I - 0.5) = 80 \times 0.5$$

$$\Rightarrow IR_3 = 40 \quad \text{--- (1)}$$

By applying KVL, we get

$$IR_3 + 20I + 10I = 100$$

$$\Rightarrow 40 + 30I = 100$$


$$\Rightarrow 30I = 60$$

$$\Rightarrow I = 2 A$$

$$\therefore R_3 = \frac{40}{2} = 20 \Omega$$

\therefore Voltage drop across R_1 is $10 \times 2 = 20 V$

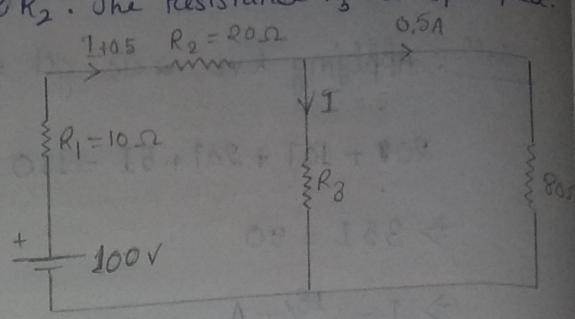Voltage drop across R_2 is $20 \times 2 = 40 V$



5) Determine equivalent resistance between terminals A and B in the following circuit.

Solⁿ By applying KVL, we get

$$V_B - 15I_1 - 35I_1 = V_A$$

$$\Rightarrow V_B - V_A = 50I_1 \quad \text{--- (i)}$$

$$\text{And, } V_B - 22I_2 - 8I_2 = V_A$$

$$\Rightarrow V_B - V_A = 30I_2 \quad \text{--- (ii)}$$

$$\text{From (i) \& (ii)} \Rightarrow 50I_1 = 30I_2$$

$$\Rightarrow I_1 = \frac{3}{5}I_2$$



$$\text{Now, } V = IR$$

$$V_B - V_A = (I_1 + I_2)R$$


$$\Rightarrow 30I_2 = \left(\frac{3}{5}I_2 + I_2\right)R$$

$$\Rightarrow 30 = \frac{8}{5}R$$

$$\Rightarrow R = 18.75\Omega$$

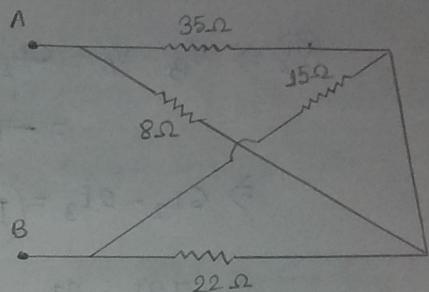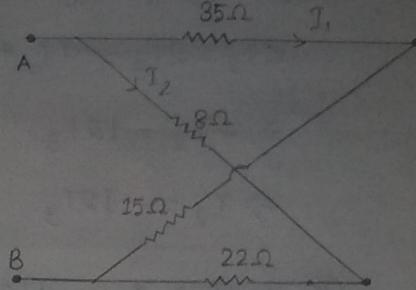

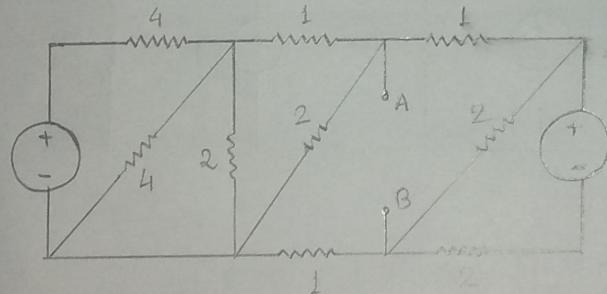6) Determine equivalent resistance between AB



By taking voltage sources as short circuit, we get

$$\text{Req between AB} = 1\Omega$$

Solⁿ By applying KCL, we get

$$4I_2 + 4I_3 = 4I_1$$


$$\Rightarrow I_1 = I_2 + I_3 \quad \text{--- (i)}$$

$$3(I_1 + I_3) + 4I_3 = 2(I_2 - I_3)$$

$$\Rightarrow 9I_3 + 3I_1 = 2I_2$$

$$\Rightarrow 9I_3 + 3I_2 + 3I_3 = 2I_2$$
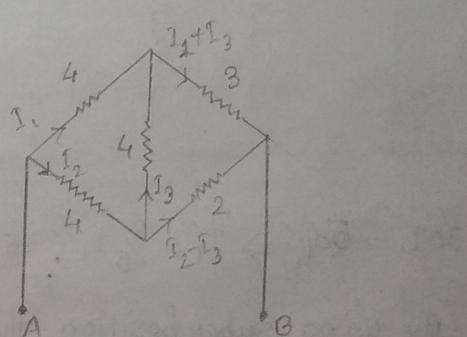
$$\Rightarrow 12I_3 + I_2 = 0 \quad \text{--- (ii)}$$



$$V_A + 4I_2 + 2(I_2 - I_3) = V_B$$

$$\Rightarrow V_B - V_A = 6I_2 - 2I_3 \quad \text{--- (iii)}$$

$$V_A + 4I_1 + 3(I_1 + I_3) = V_B$$

$$\Rightarrow V_B - V_A = 7I_2 + 10I_3 \quad \text{--- (iv)}$$

From ⑩ & ⑪, we get

$$6I_2 - 2I_3 = 7I_2 + 10I_3$$

$$\Rightarrow -I_2 = 12I_3$$

$$\Rightarrow I_2 = -12I_3$$

$$\textcircled{X} \Rightarrow \textcircled{I} \Rightarrow I_1 = -11I_3$$

$$\textcircled{X} \Rightarrow V_B - V_A = 6I_2 - 2I_3 (I_1 + I_2)R \\ = -72I_3$$

$$\Rightarrow 6I_2 - 2I_3 = (I_1 + I_2)R$$

$$\Rightarrow -72I_3 - 2I_3 = (-12 - 11)I_3 R$$

$$\Rightarrow 74 = 33R$$

$$\Rightarrow R = 74/33$$

\therefore The equivalent resistance is $74/33$



7) obtain the current I_x in the 10Ω resistor using superposition theorem.

Soln By using superposition

Theorem on 50V 1st we take


50V source and 5A will

become open circuit.

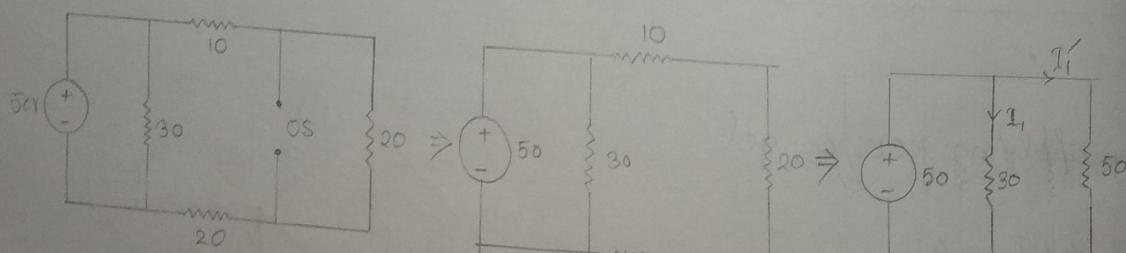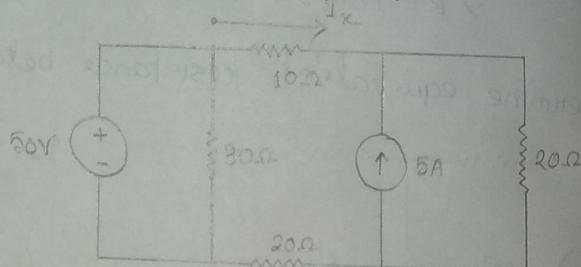

$$30I_1 = 50I'_1 \Rightarrow I'_1 = \frac{3}{5}I_1, 50I'_1 = 50 \Rightarrow I'_1 = 1A$$

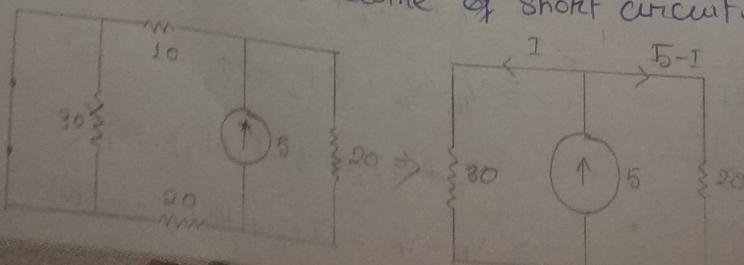By using superposition theorem on circuit we take 5A source and 50V source will become of short circuit. (Due to SC, current through 30Ω will be 0)



$$20(5-I) = 0 \text{ or } 30I$$

$$\Rightarrow 100 = 100I \text{ or } 50I$$

$$\Rightarrow I = 2A$$

By taking sign convention,


$$\begin{aligned} I_x &= I'_1 - I \\ &= 1A - 2A \\ &= -1A. \end{aligned}$$

8) Use superposition theorem and find current I .

Soln Using superposition theorem,

1st we take 5A current

Source and 25A source become

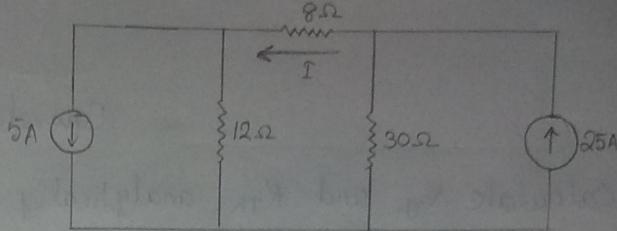

OC.

$$\begin{array}{c} \text{Circuit diagram: } 5A \downarrow \text{source, } 12\Omega, 30\Omega, 8\Omega \text{ resistor.} \\ \Rightarrow \text{Circuit diagram: } 5A \downarrow \text{source, } 12\Omega, 38\Omega \text{ (parallel branch), } 8\Omega \text{ resistor.} \\ 5 = 38I' \Rightarrow I' = \frac{5}{38} \\ 38I_1 = 12(5 - I) \\ \Rightarrow 50I_1 = 60 \\ \Rightarrow I_1 = \frac{6}{5} \text{ A} \end{array}$$

Using superposition theorem, we take 25A current source and 5A source become open circuit.



$$\begin{array}{c} \text{Circuit diagram: } 12\Omega, 30\Omega, 25A \uparrow \text{source, } 8\Omega \text{ resistor.} \\ \Rightarrow \text{Circuit diagram: } 20\Omega, 30\Omega, 25A \uparrow \text{source, } 8\Omega \text{ resistor.} \\ 30(25 - I') = 20I' \\ \Rightarrow 750 = 50I' \\ \Rightarrow I' = 15 \text{ A} \end{array}$$

∴ After taking sign convention

$$\begin{aligned} I &= I_1 + I' \\ &= \frac{6}{5} + 15 = 1.2 + 15 = 16.2 \text{ A} \end{aligned}$$

Thevenin's Theorem -

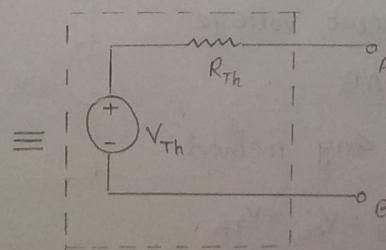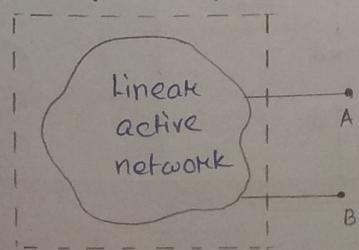
A linear active resistive network which contains one or more voltage or current sources can be replaced by a single voltage and a series resistance. The voltage is called the Thevenin's equivalent voltage (V_{Th}) and the resistance is Thevenin's equivalent resistance (R_{Th})



$V_{Th} = \text{open circuit voltage at terminals AB}$
 $R_{Th} = \text{Equivalent resistance of the network as seen from AB.}$

Equivalent circuit.

Ex

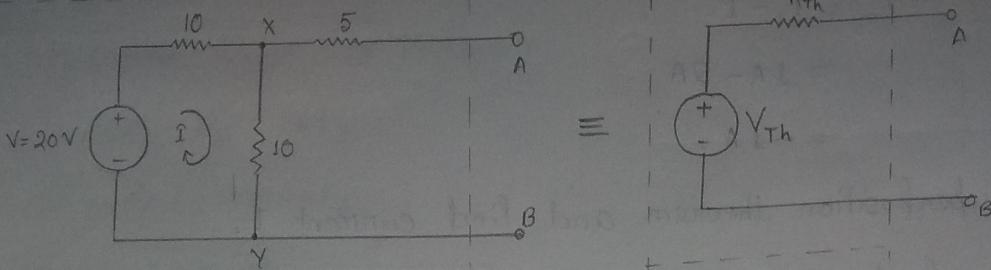

Equivalent circuit.

* Calculate V_{Th} and R_{Th} analytically


$$V_{Th} = \text{open circuit voltage across } AB = V_{xy} = I \times 10$$

$$= \frac{20}{10+10} \times 10$$

$$= 10V$$

$$R_{Th} = \text{equivalent resistance at } AB = R_{eq}$$

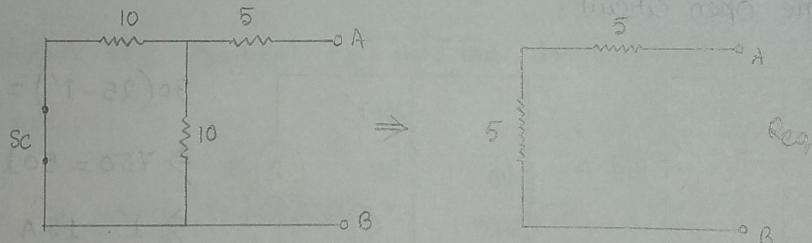
To calculate equivalent resistance across AB replace the voltage source by short circuit. The circuit becomes



$$\therefore R_{eq} = 10\Omega$$

$$\therefore R_{Th} = 10\Omega$$

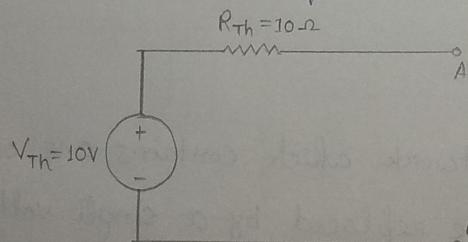So the Thvenin's equivalent circuit will be




Ex Draw Thvenin's equivalent circuit across AB

Solⁿ $V_{Th} = \text{open circuit voltage}$
across AB

We can apply any method

to find out $V_{AB} = V_{oc} = V_{Th}$.

Let's apply

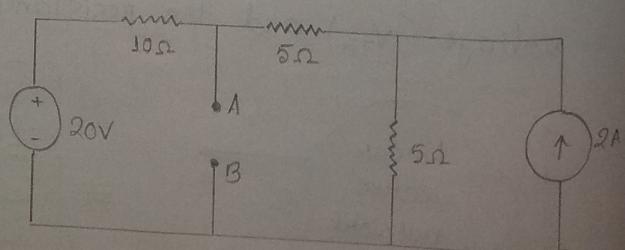

Let's apply superposition theorem.

Consider 20V source alone and

calculate current in 10Ω branch

(make the current source open)

$$I_1 = \frac{20}{20} = 1A.$$

Now, consider current source alone and

calculate current in 10Ω resistance

(make the voltage source short circuit)

Now, consider etc

Applying current division method we
can calculate current in 10Ω &
resistance due to source 2A.

$$I_1' = \frac{5}{10+5+5} \times 2A = \frac{1}{2}A.$$

\therefore Resultant current due to both sources
at 10Ω resistance is

$$I = I_1 - I_1' = 1 - \frac{1}{2} = \frac{1}{2}A \text{ (from L to R)}$$

Now, considering the original circuit

$$\text{Voltage across AB, } V_{AB} = 20V - \frac{1}{2} \times 10V \\ = 15V$$

$$\sqrt{V_{Th}} = 15V$$

Calculation of R_{Th} -

Replace voltage source by short circuit and current source by
open circuit.

Thus Thevenin's circuit will be



$$R_{Th} = 5\Omega$$

